 




**SCHOOL OF COMPUTING  
SESSION 2018/2019 SEMESTER 2  
SCSR 1013**

**SECTION-03**

**DIGITAL LOGIC PROJECT**



**FINAL REPORT**

**4-BITS XEROX MACHINE**

**Group Members:** Ridwan bin Monjur (A18CS3026)  
Nurul Ismat Tanni (A18CS4052)  
Meghla Mehnaz Rose (A18CS3017)  
Li Zhaosong(A18CS3069)

**Lecturer:** Dr. Marina Md Arshad

**Submission Date:** 18<sup>th</sup> May, 2019 (Saturday)

## DEDICATION AND ACKNOWLEDGEMENT

"Alone we can do so little; together we can do so much." – Helen Keller.

"Talent wins games, but teamwork and intelligence win championships." – Michael Jordan.

Being firm believers of these wise words, we would like to acknowledge the merits of teamwork first. If not for togetherness, this wouldn't be possible. The one person without whom we wouldn't be a team in the first place is Ms. Marina Binti Md Arshad, our Digital Logic lecturer. Therefore, we would sincerely like to thank her for her endeavours and always pushing us to think outside the box. She has guided us through every step and was always there when we needed her cooperation. We are indeed so very grateful for her guidance. All the lecturers, along with Ms Marina has given us a fulfilling university experience.

Last, but not the least, we would like to thank our family and friends who constantly support us to get through all adversities. Nonetheless, without them we wouldn't be where we are.

Needless to say, this is dedicated to our family, friends and all our lecturers, specially Ms. Marina Binti Md Arshad.





**Nurul's Family**



**Li's Family**



**Rose's Family**



**Ridwan's Family**

# TABLE OF CONTENTS

| <b><i>CONTENTS</i></b>                              | <b><i>PAGE NUMBER</i></b> |
|---|---------------------------|
| <u>Our Goals</u> .....                              | 4                         |
| <u>Introduction</u> .....                           | 5                         |
| <u>DEEDS Diagram</u> .....                          | 6                         |
| <u>4-Bit Design with K-maps and Equations</u> ..... | 7                         |
| <u>4-Bit Design with K-maps and Equations</u> ..... | 8                         |
| <u>4-Bit Design with K-maps and Equations</u> ..... | 9                         |
| <u>4-Bit Design with K-maps and Equations</u> ..... | 10                        |
| <u>Enhancement</u> .....                            | 11                        |
| <u>Enhancement</u> .....                            | 12                        |
| <u>Enhancement</u> .....                            | 13                        |
| <u>Enhancement</u> .....                            | 14                        |
| <u>Block diagram</u> .....                          | 15                        |
| <u>Final DEEDS circuit</u> .....                    | 16                        |
| <u>Instructions of Using the Machine</u> .....      | 17                        |
| <u>References</u> .....                             | 18                        |
| <u>Appendices</u> .....                             | 19                        |

## OUR GOALS

The project incorporates few objectives that were needed to be fulfilled. It was a step-by-step procedure. At our first day, 7th May, 2019, our aim was to type the code, compile it, burn it and at last test it. The simple xerox machine controller implemented 3 different components on a single PLD device. They are count-up counter, comparator, input switches and decoder (Pattern detector)—Clock enabler. This was part 1: 2-bit Xerox Machine Circuit testing.

The description of the first part functions are described below:

- *Input switches*-It is needed to enter the user's required number of copies. It will be connected to the comparator to be compared with the count-up counter.
- *Comparator*-The comparator compares the input number of copies of paper if it is equal to the current number of printed pages.
- *Count-up counter*-This is needed to count up the number of pages needed to copy. The counter will send the output to the comparator until it matches with the number entered. A 3-bits counter was created and built with aid of the state diagram, truth table and K-map and then finally an equation was obtained.
- *Clock Enabler/disabler*-Clock enabler/disabler is needed to stop the process of the counter or to saturate the counter. It is needed to check if all the requirements are satisfied by the comparator or not. It can also check if the start button is on or off.



Next, part 2 comprised of the xerox machine enhancement in DEEDS stimulator. We implemented the design using DEEDS software. Furthermore, we had to extend the design with the other components, such as encoder, comparator etc.

## INTRODUCTION

After being assigned to our respective groups, we first discussed our ideas in our activity room. And, that very day started working in our block diagram. (It will be provided in the upcoming pages). After that, we went to Ms Marina with our draft diagram and she helped us correct it and enhance it in order to have a more eligible and efficient one. In the upcoming pages we will be describing all our procedures—from state diagrams to K-Map. And, how we landed in our final result.

Our method of working was doing all the steps together with every member's consent. However, we also used our strengths and divided a few tasks that way. Ridwan and Li, being good at technicals, brought the ideas in the form of K-map and state diagrams. While Nurul and I(Rose), improvised on what they did and used our decorative skills to write the group report. Ridwan and Li helped too in that as well. Even though tasks were divided, we all helped each other when needed.




**Pictures of us during discussion and consultation**



# DEEDS DIAGRAM

***Fig. 1 V: Screenshot of the 2-bits Deeds Diagram***

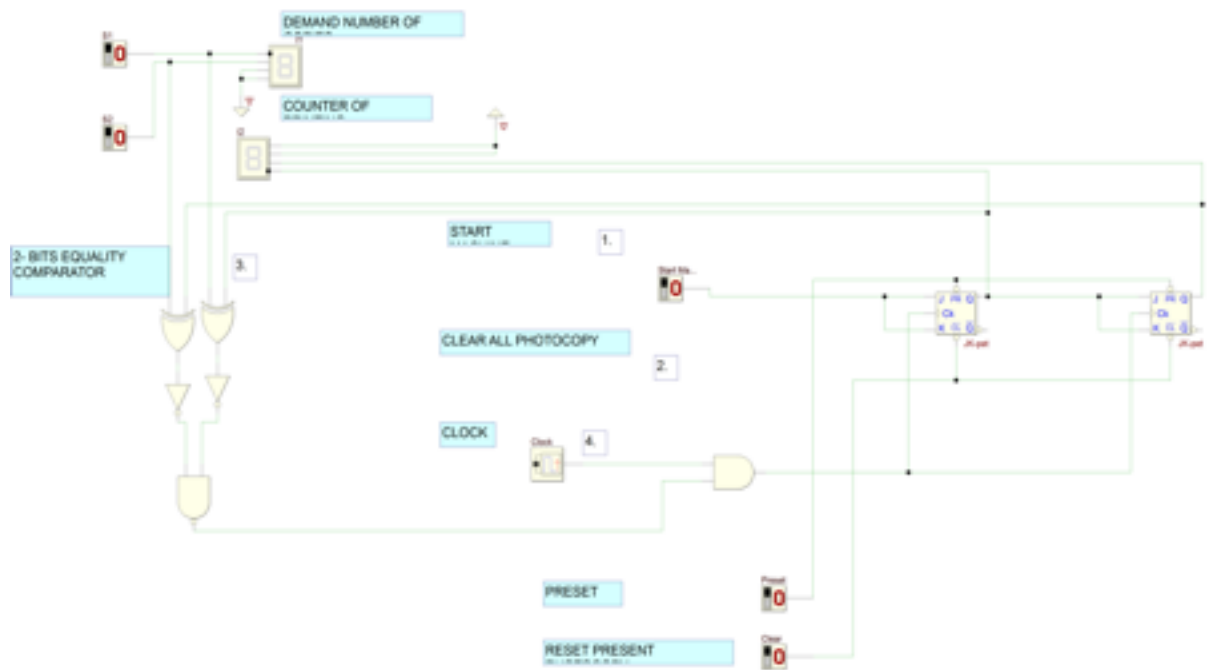

## 4-BIT DESIGN WITH K-MAP AND EQUATIONS



| Present State |    |    |    | Next State |         |         |         | JK Transition Table |    |    |    |    |    |    |    |
|---------------|----|----|----|------------|---------|---------|---------|---------------------|----|----|----|----|----|----|----|
| Q3            | Q2 | Q1 | Q0 | Q3<br>+    | Q2<br>+ | Q1<br>+ | Q0<br>+ | J3                  | K3 | J2 | K2 | J1 | K1 | J0 | K0 |
| 0             | 0  | 0  | 0  | 0          | 0       | 0       | 1       | 0                   | X  | 0  | X  | 0  | X  | 1  | X  |
| 0             | 0  | 0  | 1  | 0          | 0       | 1       | 0       | 0                   | X  | 0  | X  | 1  | X  | X  | 1  |
| 0             | 0  | 1  | 0  | 0          | 0       | 1       | 1       | 0                   | X  | 0  | X  | X  | 0  | 1  | X  |
| 0             | 0  | 1  | 1  | 0          | 1       | 0       | 0       | 0                   | X  | 1  | X  | X  | 1  | X  | 1  |
| 0             | 1  | 0  | 0  | 0          | 1       | 0       | 1       | 0                   | X  | X  | 0  | 0  | X  | 1  | X  |
| 0             | 1  | 0  | 1  | 0          | 1       | 1       | 0       | 0                   | X  | X  | 0  | 1  | X  | X  | 1  |
| 0             | 1  | 1  | 0  | 0          | 1       | 1       | 1       | 0                   | X  | X  | 0  | X  | 0  | 1  | X  |
| 0             | 1  | 1  | 1  | 1          | 0       | 0       | 0       | 1                   | X  | X  | 1  | X  | 1  | X  | 1  |
| 1             | 0  | 0  | 0  | 1          | 0       | 0       | 1       | X                   | 0  | 0  | X  | 0  | X  | 1  | X  |
| 1             | 0  | 0  | 1  | 1          | 0       | 1       | 0       | X                   | 0  | 0  | X  | 1  | X  | X  | 1  |
| 1             | 0  | 1  | 0  | 1          | 0       | 1       | 1       | X                   | 0  | 0  | X  | X  | 0  | 1  | X  |
| 1             | 0  | 1  | 1  | 1          | 1       | 0       | 0       | X                   | 0  | 1  | X  | X  | 1  | X  | 1  |
| 1             | 1  | 0  | 0  | 1          | 1       | 0       | 1       | X                   | 0  | X  | 0  | 0  | X  | 1  | X  |
| 1             | 1  | 0  | 1  | 1          | 1       | 1       | 0       | X                   | 0  | X  | 0  | 1  | X  | X  | 1  |
| 1             | 1  | 1  | 0  | 1          | 1       | 1       | 1       | X                   | 0  | X  | 0  | X  | 0  | 1  | X  |
| 1             | 1  | 1  | 1  | 0          | 0       | 0       | 0       | X                   | 1  | X  | 1  | X  | 1  | X  | 1  |

J3

| Q3Q2 \ Q1Q0 | 00 | 01 | 11 | 10 |
|-------------|----|----|----|----|
| 00          | 0  | 0  | 0  | 0  |
| 01          | 0  | 0  | 1  | 0  |
| 11          | X  | X  | X  | X  |
| 10          | X  | X  | X  | X  |

0111

1111

J3=Q2Q1Q0

J2

| Q3Q2 \ Q1Q0 | 00 | 01 | 11 | 10 |
|-------------|----|----|----|----|
| 00          | 0  | 0  | 1  | 0  |
| 01          | X  | X  | X  | X  |
| 11          | X  | X  | X  | X  |
| 10          | 0  | 0  | 1  | 0  |



0011

0111

1111

1011

---

$J_2 = Q_1Q_0$

$J_1$

| $Q_3Q_2 \backslash Q_1Q_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00                         | 0  | 1  | X  | X  |
| 01                         | 0  | 1  | X  | X  |
| 11                         | 0  | 1  | X  | X  |
| 10                         | 0  | 1  | X  | X  |

0001

0101

1101

1001

0011

0111

1111

1011

---

$J_1 = Q_0$

$J_0$

| $Q_3Q_2 \backslash Q_1Q_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00                         | 1  | X  | X  | 1  |
| 01                         | 1  | X  | X  | 1  |
| 11                         | 1  | X  | X  | 1  |
| 10                         | 1  | X  | X  | 1  |

$J_0 = 1$

$K_3$

| $Q_3Q_2 \backslash Q_1Q_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00                         | X  | X  | X  | X  |
| 01                         | X  | X  | X  | X  |
| 11                         | 0  | 0  | 1  | 0  |
| 10                         | 0  | 0  | 0  | 0  |

0111

1111

---

K3=Q2Q1Q0

K2

| Q3Q2 \ Q1Q0 | 00 | 01 | 11 | 10 |
|-------------|----|----|----|----|
| 00          | X  | X  | X  | X  |
| 01          | 0  | 0  | 1  | 0  |
| 11          | 0  | 0  | 1  | 0  |
| 10          | X  | X  | X  | X  |

0011

0111

1111

1011

---

K2=Q1Q0

K1

| Q3Q2 \ Q1Q0 | 00 | 01 | 11 | 10 |
|-------------|----|----|----|----|
| 00          | X  | X  | 1  | 0  |
| 01          | X  | X  | 1  | 0  |
| 11          | X  | X  | 1  | 0  |
| 10          | X  | X  | 1  | 0  |

0001

0101

1101

1001

0011

0111

1111

1011


---

K1=Q0

|      |      |    |    |    |    |
|------|------|----|----|----|----|
| K0   |      |    |    |    |    |
|      | Q1Q0 | 00 | 01 | 11 | 10 |
| Q3Q2 |      |    |    |    |    |
| 00   |      | X  | 1  | 1  | X  |
| 01   |      | X  | 1  | 1  | X  |
| 11   |      | X  | 1  | 1  | X  |
| 10   |      | X  | 1  | 1  | X  |

K0=1



 


## 2. Identical comparators and counters (give HIGH logic output):

- 1) Comparator 1 for Counter 1: compares number of **sets of photocopy** with the count by Counter1.
- 2) Comparator 2 for Counter 2: compares **number of pages of photocopy for each set** with the count by Counter2.

### 3) Enhanced function 3: Two Clock Enablers

 
- 1) Clock enabler 1/ Clock enabler for Counter 1 (Number of sets)



- This clock is **not** driven by a clock generator. It is driven by the '1' / HIGH output of the AND.


- Bottom wire into the AND gate comes from the **Comparator 2**. If the number of pages for each set of photocopy are same as user inputted, then Comparator 2 gives '1' / HIGH logic. This HIGH logic increments **Counter 2**.
- Top wire into the AND gate comes from the **comparator 1** (for number of sets).
  - There is a NOT gate which means if Comparator 1 gives HIGH output, it will stop the clock *because NOT inverses the HIGH output to LOW output*.
  - Comparator 1 gives HIGH output if all the number of sets have been completed.
  - If number of sets of photocopy is completed, the task is over, so we want to stop it now by the NOT gate.

 2) Clock enabler 2/ Clock enabler for Counter 2 (Number of pages for each set)



- Bottom wire into the AND gate comes from the **password**, giving logic '0' / stopping clock for **Counter 2 (Number of pages for each set)** if password fails.
- Top wire into the AND gate comes from the **comparator 1** (for number of sets), which stops clock if number of sets equal.

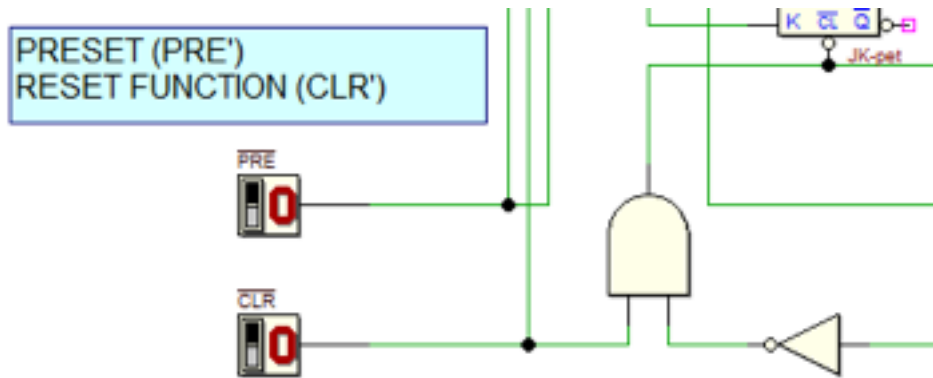
4. **Enhanced Function 3: Clear counter2 when one set of photocopy is completed.**



When RESET=1:

- 1) Left wire is coming from RESET switch ('1' at moment).
- 2) Right wire is coming from **Comparator2**. When one set of photocopy is completed, it gives '1'/HIGH output. We inverse it, so '0' goes into the AND.
- 3) AND gives RESET=0. So, counter resets.

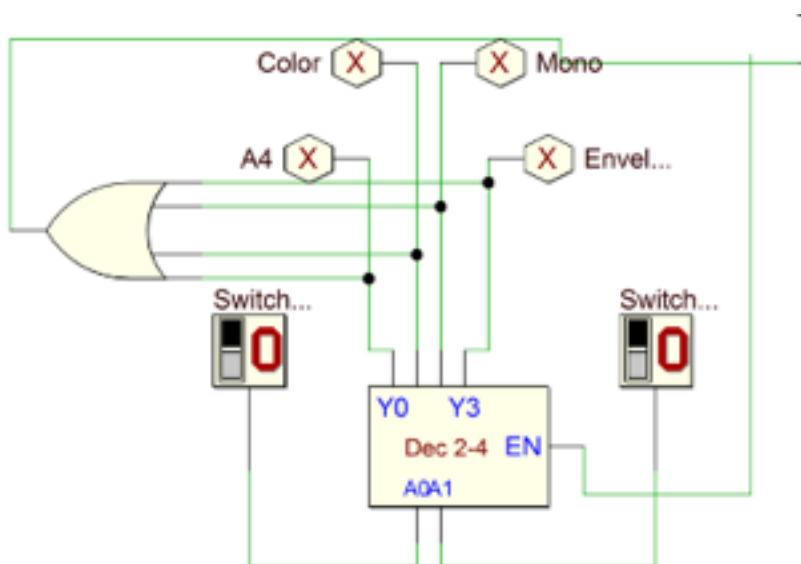
#### 4) Enhanced Function 4: Type of Photocopy




User can choose any of the two paper types and any of the two colour options.



## BLOCK DIAGRAM

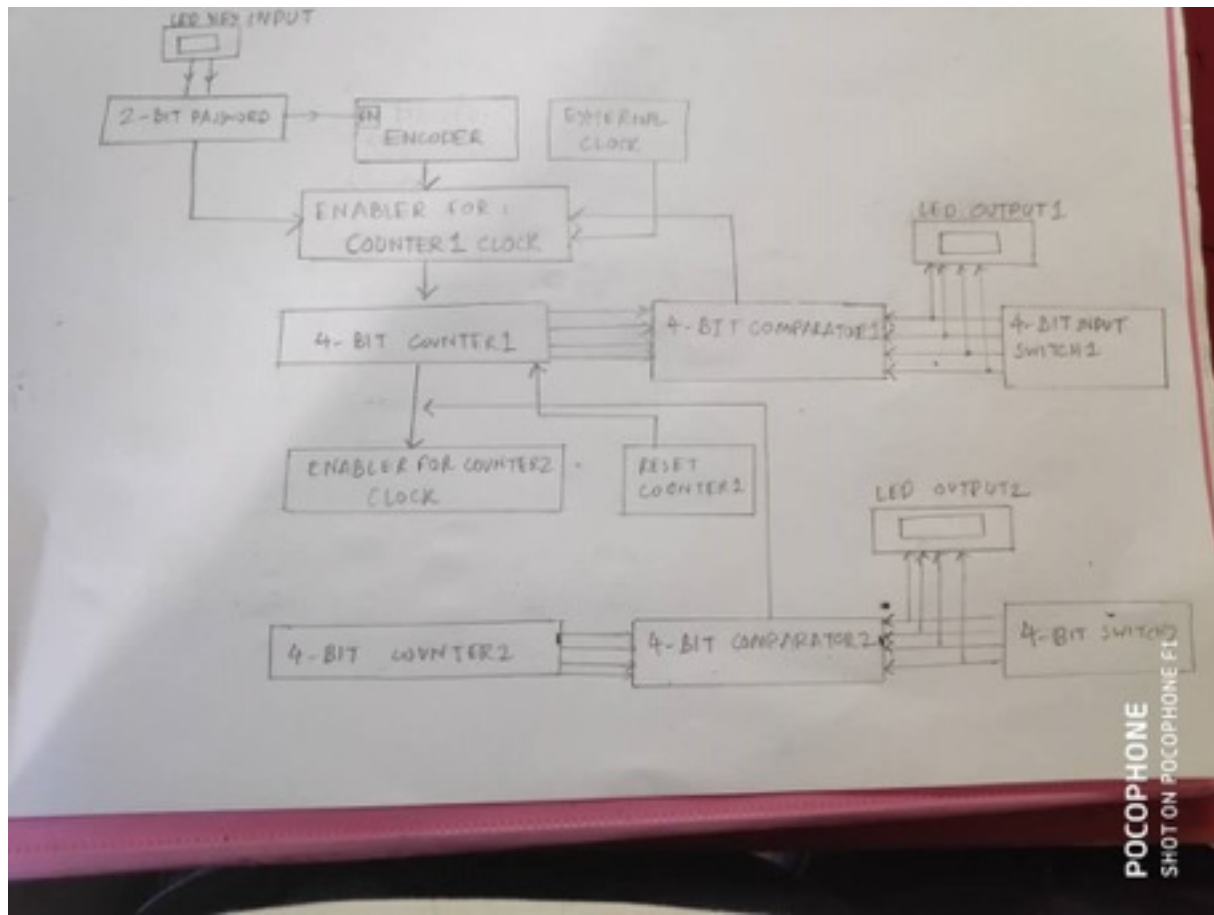

# FINAL DEEDS CIRCUIT

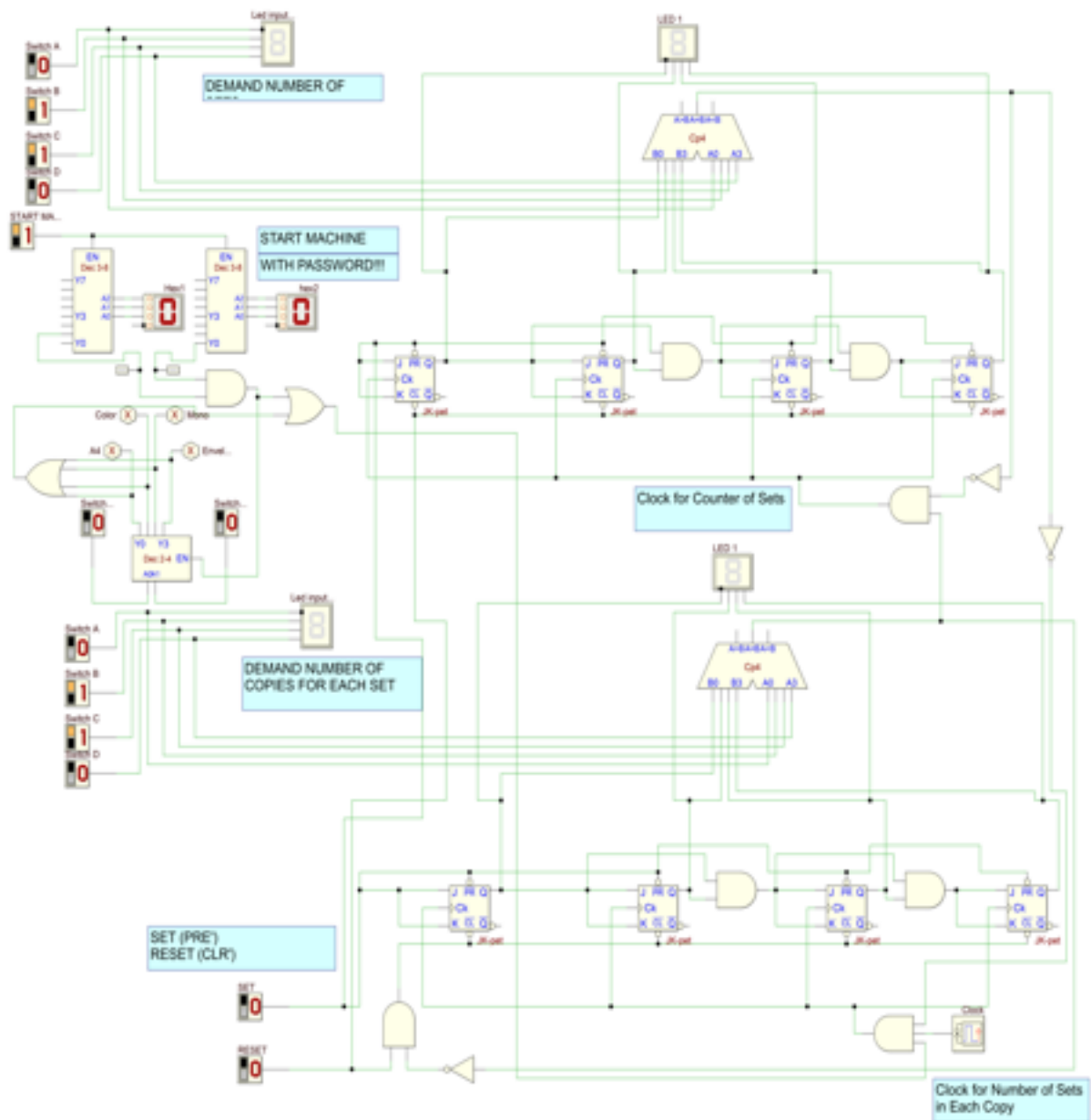

## INSTRUCTIONS OF USING THE MACHINE:

1. Switch on START MACHINE.
2. Switch on  
  
PRE'=1  
  
CLR'=1
3. Set Password: '2 O' i.e. Left hex digit should be '2'
4. (Optional) Choose your photocopy type: a) Colour or Mono? AND b) A4 or A3?
5. Choose the number of sets and number of pages for each set.
6. Enjoy! Just press the clock.

## REFERENCES

- Digital Fundamentals by Thomas L. Floyd, 11 edition
- Fundamentals of Logic Design, Sixth Edition, Charles H. Roth, Larry L. Kenney
- Digital Logic, School of Computing, Faculty of Engineering, University Teknologi Malaysia
- <https://www.electronics-tutorials.ws>
- <https://www.allaboutcircuits.com/textbook/digital/chpt-10/j-k-flip-flop/>
- <https://electronics.stackexchange.com/questions/323093/what-is-the-difference-between-enable-and-clock-in-flip-flops>
- Marina, M. A. (2017). Report Format: REPORT for DIGITAL LOGIC PROJECT. Johor: Marina Md Arshad, Department of Computer Science, Faculty of Computing.

# Appendices

## Software used;

- DEEDS software.
- Win CULP.
- Wellon.

**Lab hours:** 5 hours

## Project group members:

- Meghla Mehnaz Rose
- Ridwan Bin Monjur
- Nurul Ismat Tanni
- Li Zhaosang

## Project supervisor:

Miss Marina Binti Mad Arshad.

